
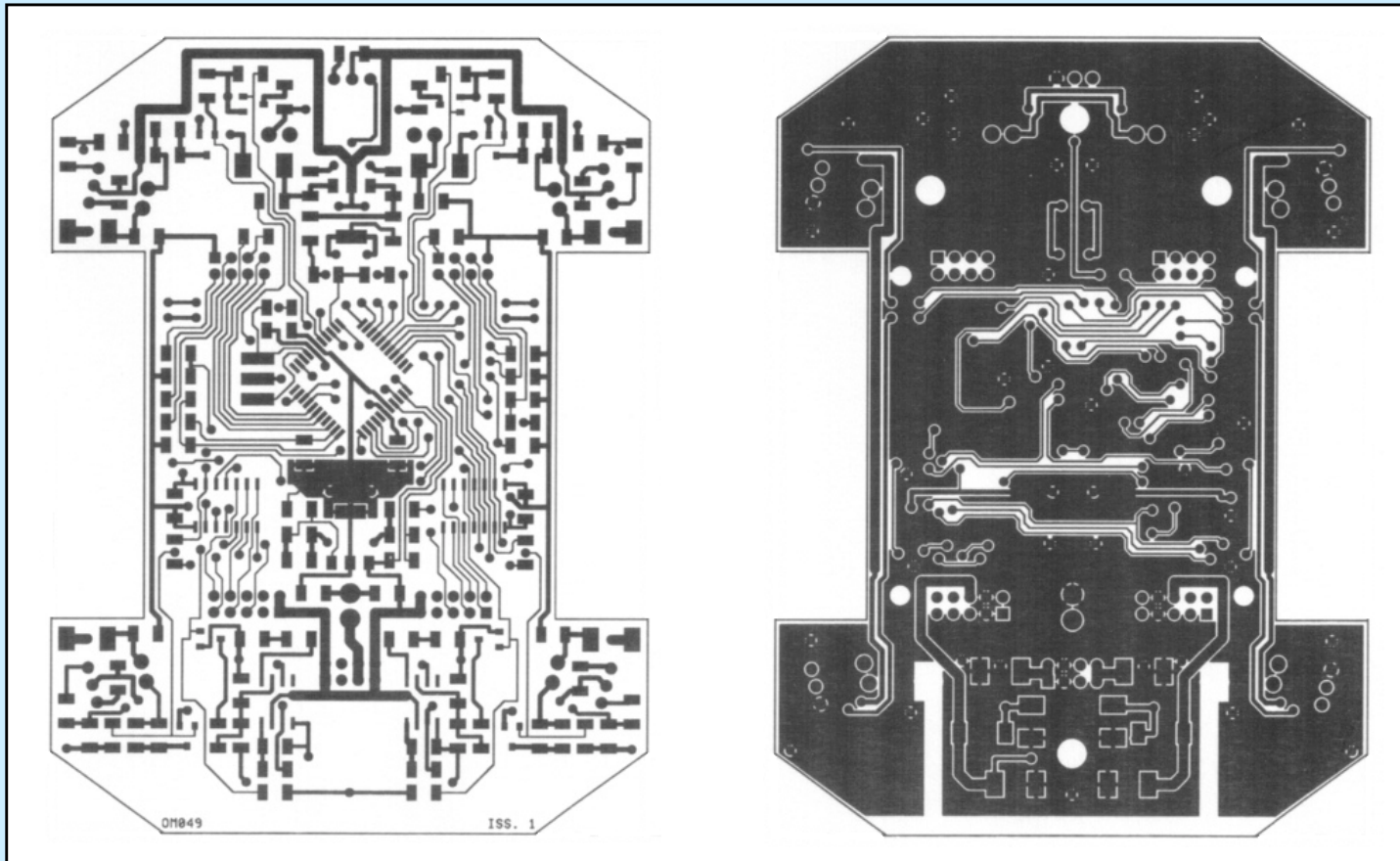


Power & Ground Systems

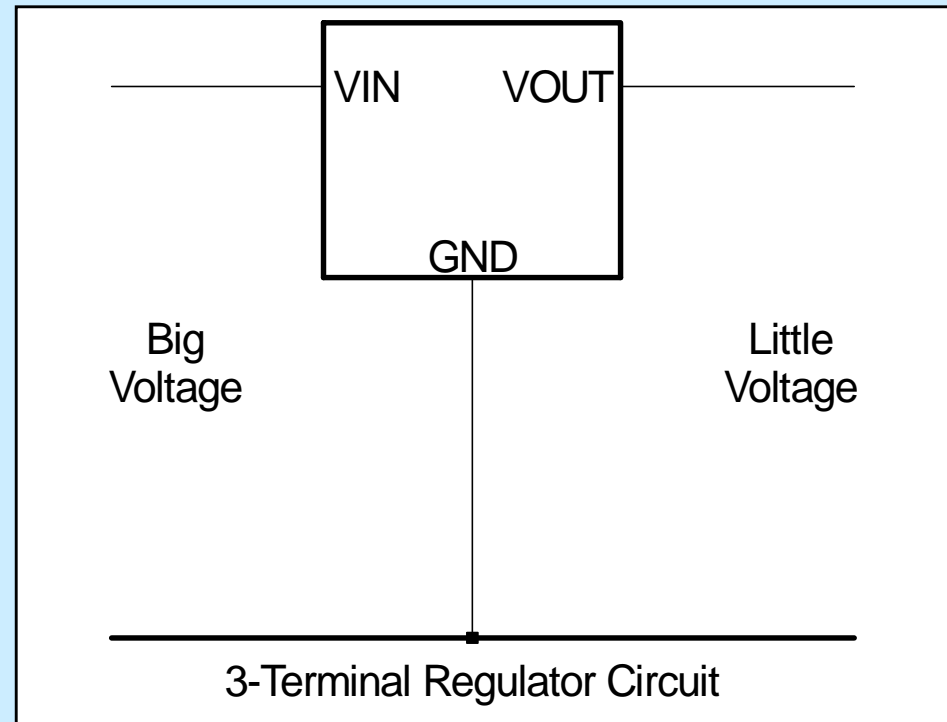

a few tips on getting it right...er

Surely - Isn't It Just One of These?



You Might be Right! But Let's See ...

Introduction

A Good Power and Ground System is essential for:-


- Circuit Reliability
- Accuracy of Measurements
- Measurement Repeatability
- Low-Noise
- Efficiency

Yet, despite all these benefits, consideration is often only given to this subject once all the 'interesting' stuff is complete!

So in the hope of designing better circuits we'll look at:-

- What Makes a 3-Terminal Regulator Tick
- Useful Devices from a few Popular Families
- Some Regulator Application Considerations
- Some PCB Layout Ideas


Basic Series Regulator

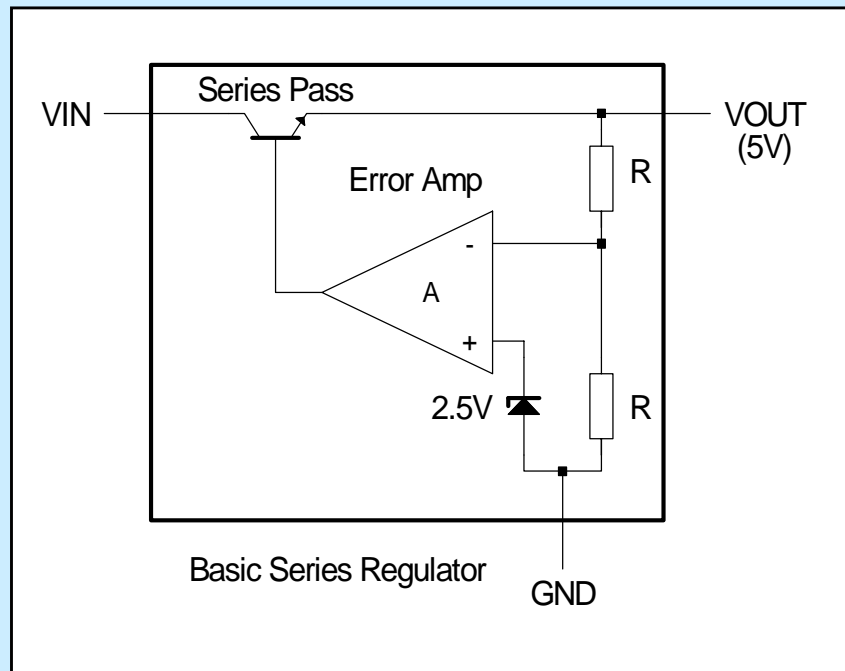


Simplified Internal Block Diagram of a typical 3-Terminal Regulator

- $V_{IN} > V_{OUT}$
- Series Pass device does all the hard work
- Error Amplifier compares V_{OUT} with Reference
(Attempts to equalise its Input Voltages)
- Ratio of 2 Resistors sets Output Voltage
(If Rs are same value: $V_{OUT} = 2 \times V_{REF}$)

Basic Series Regulator

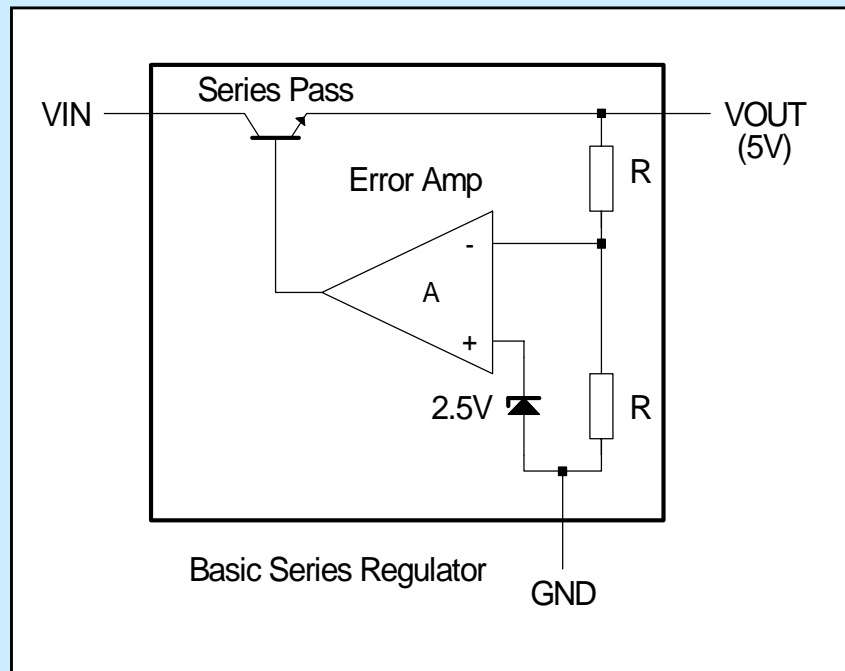

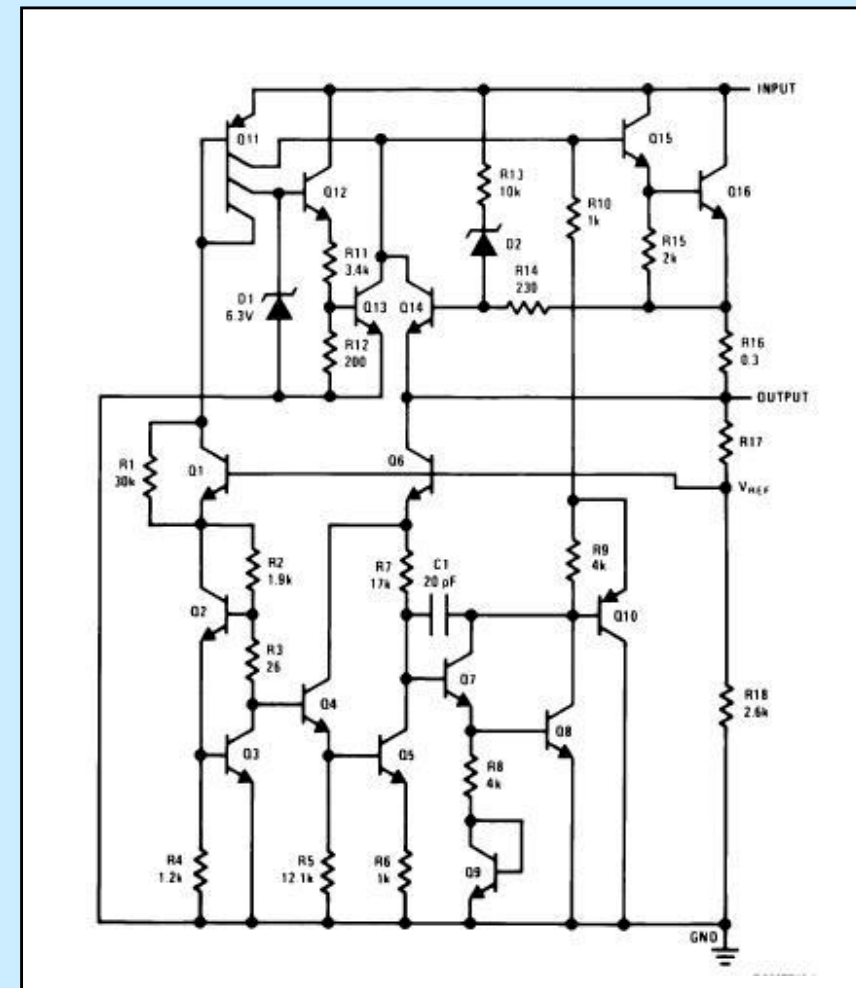- Series Pass Device - Q15/Q16
- Error Amplifier - Q7/Q8/Q10
- Reference Diode - Q7/Q8
- Short Cct Protection - Q14/R16
- Output Voltage Set - R17/R18



LM78xx Family - Internal Circuit

Useful Regulator Types

High Power Regulators:- $I_{OUT} > 1A$

- LM78xx Series Fixed Voltage - Standard Drop-Out
- LM317 Adjustable Voltage - Standard Drop-Out
- LM2940 Series Fixed Voltage - Low Drop-Out

All the above are available in various TH and SMD packages

Low Power Regulators:- $I_{OUT} < 1A$

- LM1117 Series Fixed & Adjustable Voltage - Semi LDO
- LP2980 Series Fixed Voltage - Low Drop-Out

LM1117 available in various TH and SMD packages - LP2980 only in SOT23-5

The LM78xx Family

Advantages :-

Very Simple to Use

Needs 'no' External Components

C_{in} needed if reservoir capacitor is remote - > 50mm

C_{out} reduces high frequency output noise

Preset Output Voltages (5V, 12V, 15V)

Available in Negative Output Form - LM79xx

Available in Low-Power Version - LM78Lxx

Cheap as Chips

Disadvantages :-



Not Low Drop-Out - at least 1.5V

Output Accuracy not Special at $\pm 4\%$

No Adjustable Version

Significant Quiescent Current - about 8mA

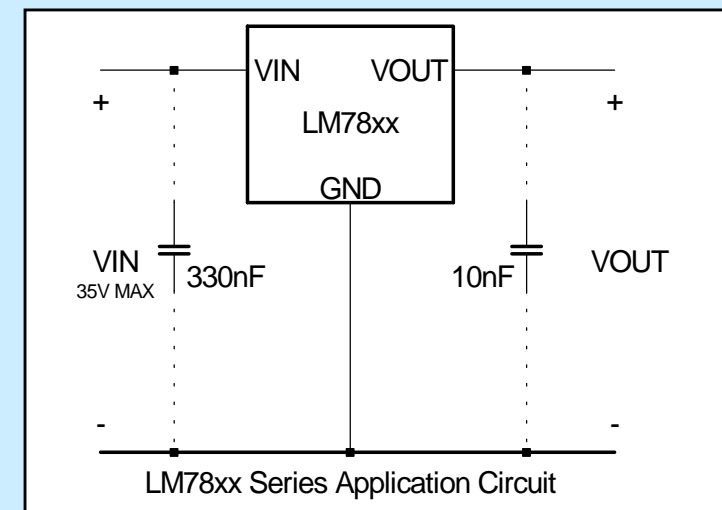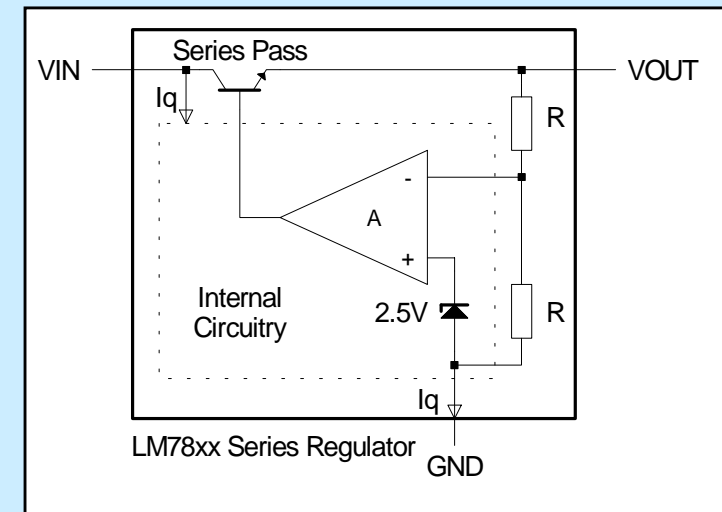Quiescent Current flows to Ground - Wasted



The LM317 Family

Advantages :-

Simple to Use

Adjustable Output Voltage - 1.25V to 37V

$$V_{OUT} = 1.25V \times (1 + R2/R1) + (I_{ADJ} \times R2)$$

If $I_{MIN} \gg I_{ADJ}$ then $V_{OUT} = 1.25V \times (1 + R2/R1)$

Available in Low-Power Version - LM317L

Quiescent Current flows to Output Pin

Low Adjustment Pin ('GND') Current - 50uA

Cheap as Chips

Disadvantages :-



Not Low Drop-Out - at least 1.5V

Output Accuracy not Special at $\pm 4\%$

But you can trim it if R2 is made variable

Needs 2 Resistors to set Output Voltage

No Negative Output Version

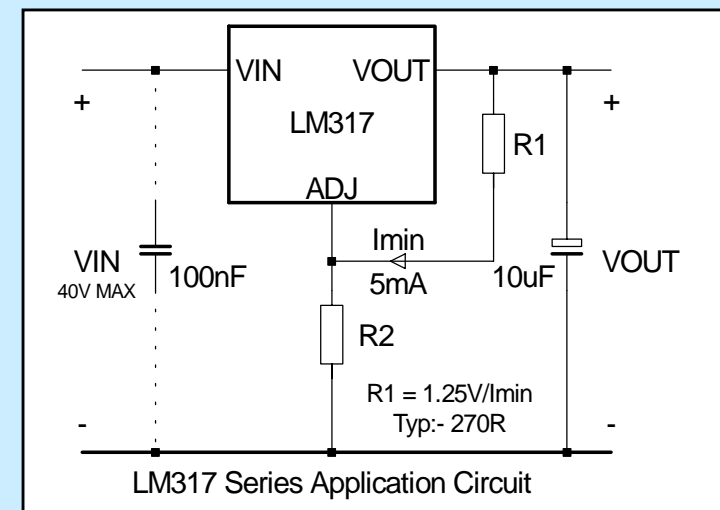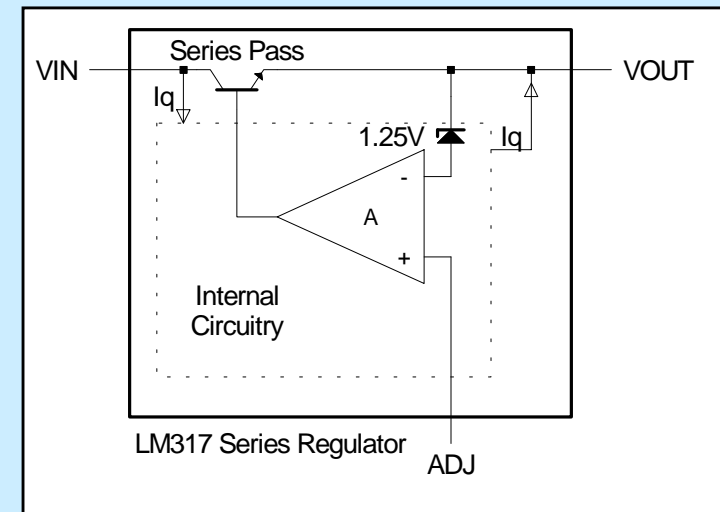

The LM1117 Family

Advantages :-

Simple to Use

Semi Low Drop-Out Voltage - about 1V

Available in Fixed and Adjustable Versions

Fixed Versions provide 1.8V, 2.5V, 3.3V and 5V

Adjustable Version can be set over 1.25V to 14V
(VOUT equations same as for LM317)

Quiescent Current flows to Output Pin

Output Accuracy not Bad at $\pm 2\%$



Disadvantages :-

Low Maximum Input Voltage - 18V

Needs 2 Resistors to set Output Voltage

COUT ESR Specification Tight

No Negative Output Version

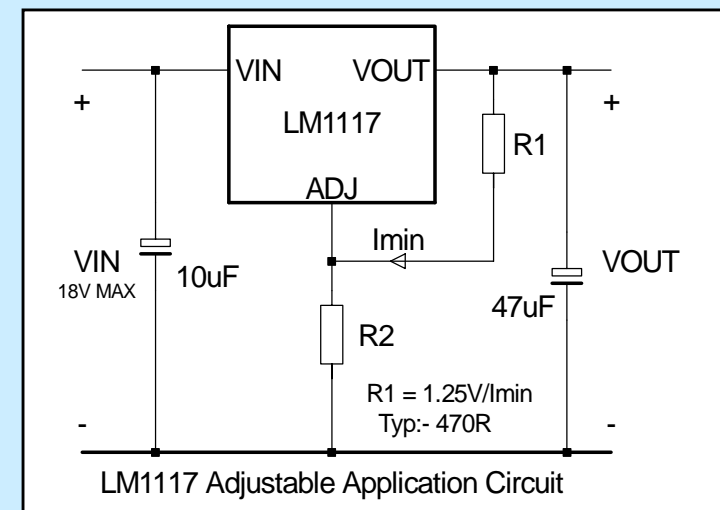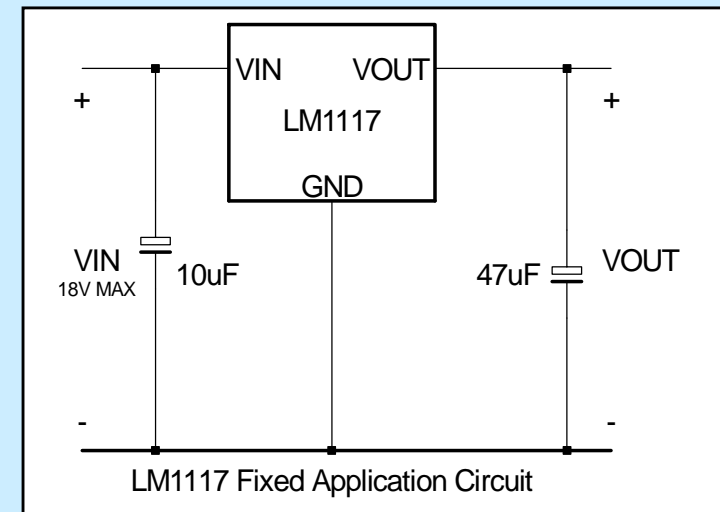



The LP2980 Family

Advantages :-

- Simple to Use
- Very Low Drop-Out Voltage - 0.1V @ 50mA
- Preset Output Voltages (3.0V, 3.3V, 5.0V)
- Low Quiescent Current - flows to GND Pin
- Output Accuracy not Bad at $\pm 1.5\%$
- Fast Transient Response
- Shutdown Capability
- Small Size - SOT23-5 Package

Disadvantages :-

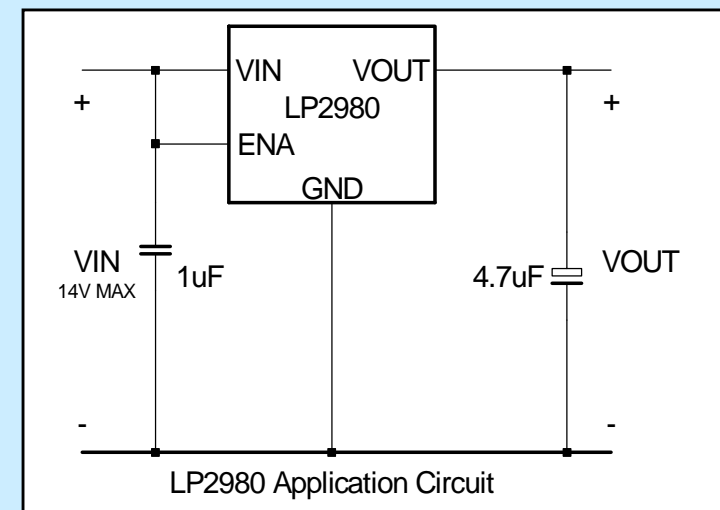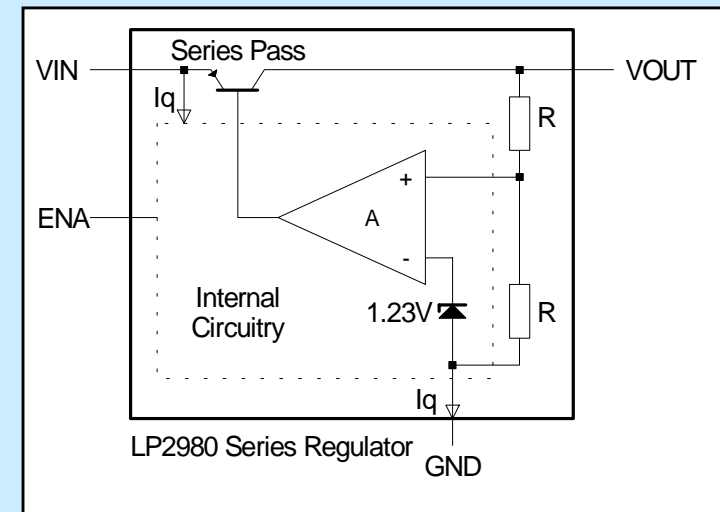- Low Maximum Input Voltage - 14V
- COUT ESR Specification Tight
- Only Suitable for Low Current Use <50mA




Voltage Regulator Considerations

Using 3-Terminal Regulators is not always Straightforward.
Problem Areas Can be:-

- Drop-Out Voltage
- Minimum Load Current
- Load Regulation
- Transient Response
- Output Capacitor ESR on LDOs
- Ground Current
- Thermal Management

Regulator Drop-out Voltage

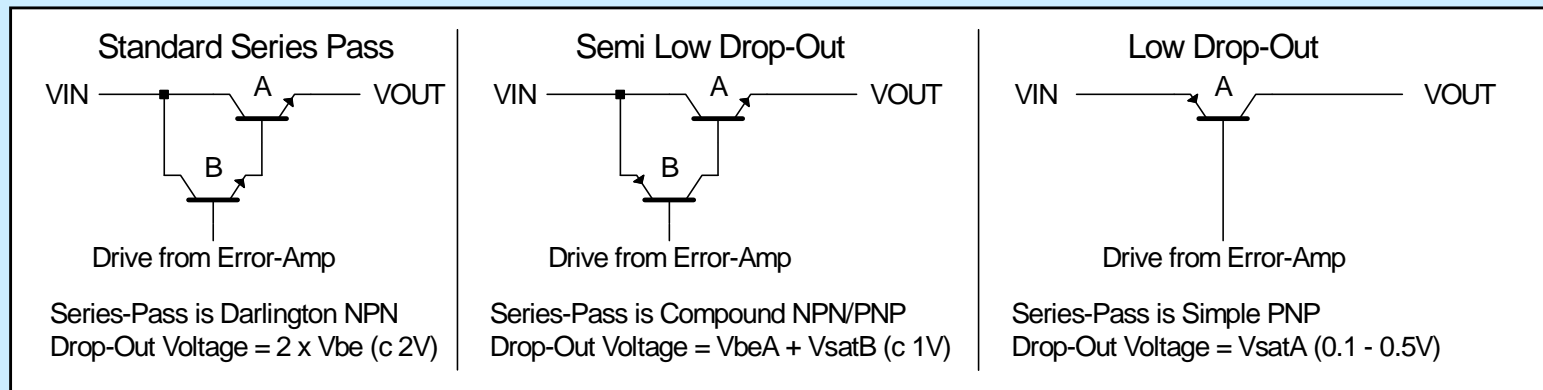


Standard Series Pass

- High Gain - Low Drive Current
- Driver Current (B) flows to Output
- Lowest 'Ground Current' (< 10mA)
- Highest Drop-Out Voltage - up to 2.5V
- Highest Minimum Power Dissipation
- Relaxed De-coupling Requirements
- Lowest Cost


Low Drop-Out

- Low Gain - High Drive Current
- Driver Current (A) flows to Ground
- Highest 'Ground Current' (up to 50mA)
- Lowest Drop-Out Voltage - maybe 50mV
- Lowest Minimum Power Dissipation
- Strict De-coupling Requirements
- Highest Cost

Regulator Drop-out Voltage

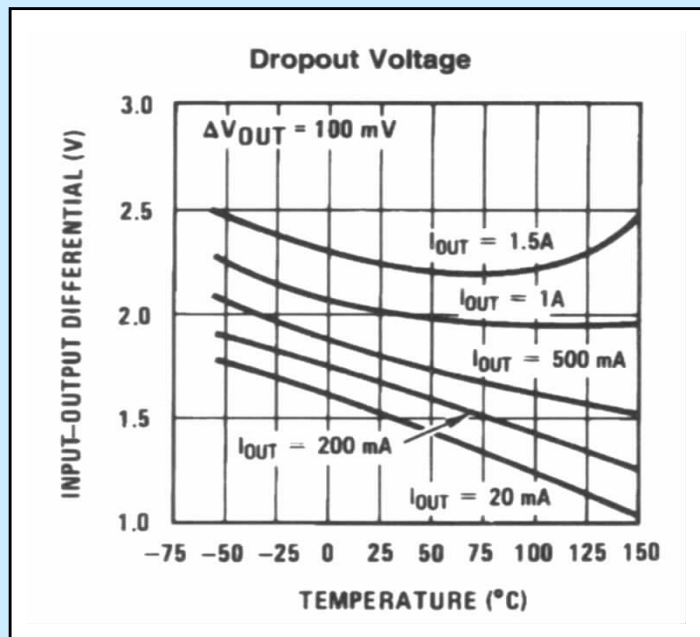

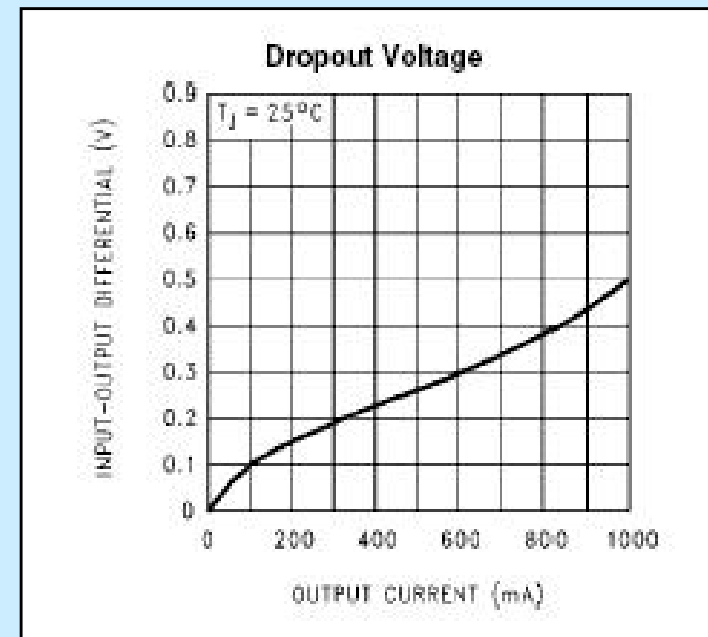Standard Regulator - LM317
 $V_{DO} @ 0.5A = 1.75V (25^\circ C)$



Low Drop-Out Regulator - LM2940
 $V_{DO} @ 0.5A = 0.25V (25^\circ C)$



Note that Drop-Out Voltage is typically specified at 'd Vout' 100mV
 Regulator Output will begin to fall from its Nominal Value at a
 larger Input-Output Differential than indicated on the Graphs

Minimum Load Current

- Not a Problem with Regulators that 'waste' their I_q to Ground
- For Regulators that return I_q to V_{OUT} we MUST provide a Load
 - it's got to go somewhere!
 - without an adequate 'sink' V_{OUT} will rise above the set output voltage

So why use this Type?

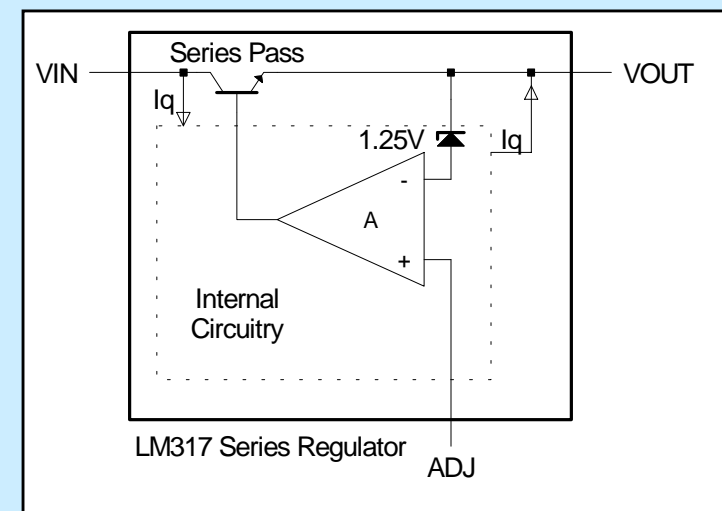
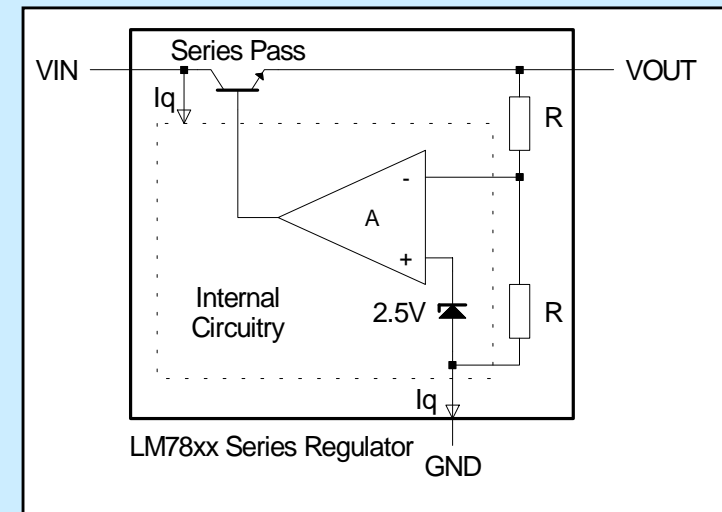
- Adjustable Output is useful for Odd V_{OUT}
- We can make a small efficiency saving



Minimum Load Current


- Standard Application wastes I_q to GND
 - No real benefit over LM78xx
- Hi-efficiency Circuit wastes only 1mA
 - Needs a Minimum Load-Circuit Current
 - I_{LOAD} MUST ALWAYS be at least 4mA
 - Not a problem in most Mouse circuits
 - Microprocessor, Logic ICs and General Circuitry
 - Has an easy approximate V_{OUT} calculation
 - $V_{OUT} = 1.25V + R_2 mV - (R_2 \text{ value in ohms})$

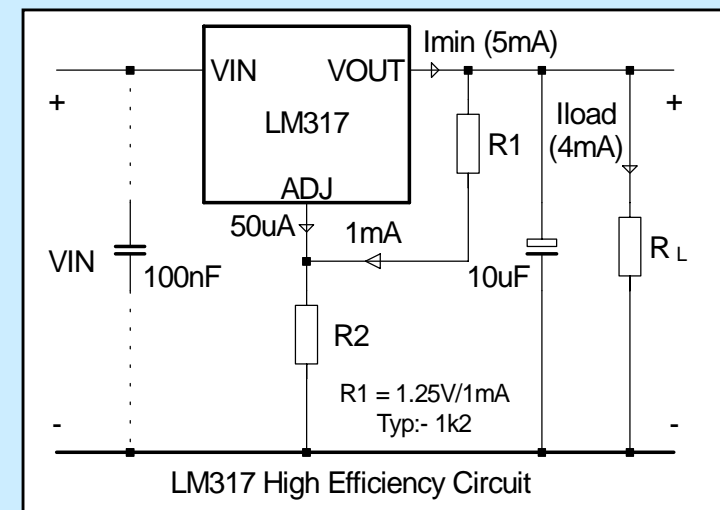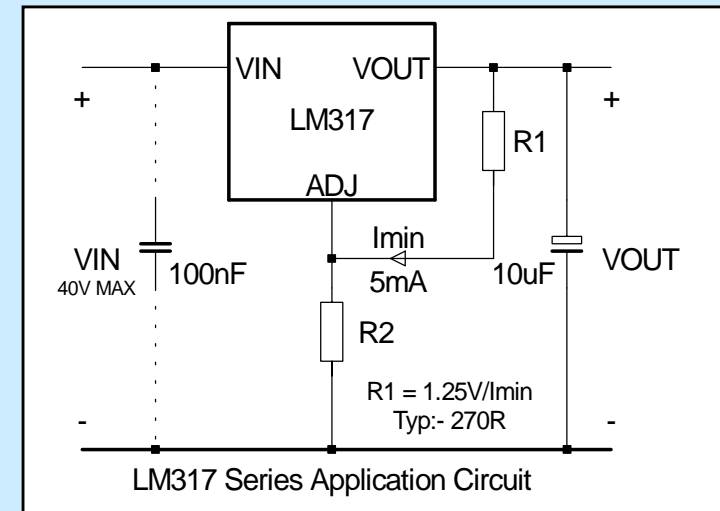Note: if I_{LOAD} can fall below 4mA then increase I_{R1}



Load Regulation


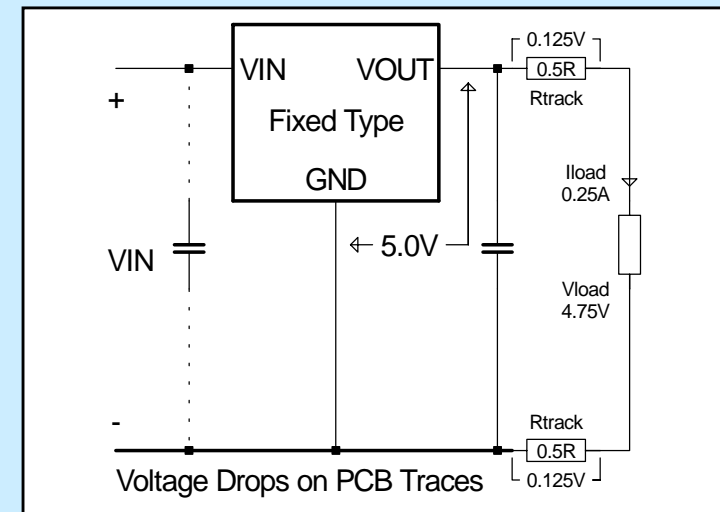
- Regulators define V_{OUT} at Output
Fixed Output Types:- V_{OUT} to GND
Adjustable Types:- V_{OUT} to 'R2 -ve' (0V)
- PCB Traces can cause Volt-Drops due to their Resistance
- Even at Modest Load Currents the Drops can be significant:-
Combination of 2 x 0.5R Track Resistance and 0.25A Load Current reduces effective supply voltage by 0.25V
- This is enough to cause Trouble!



Load Regulation

Reducing PCB Voltage Drops:-

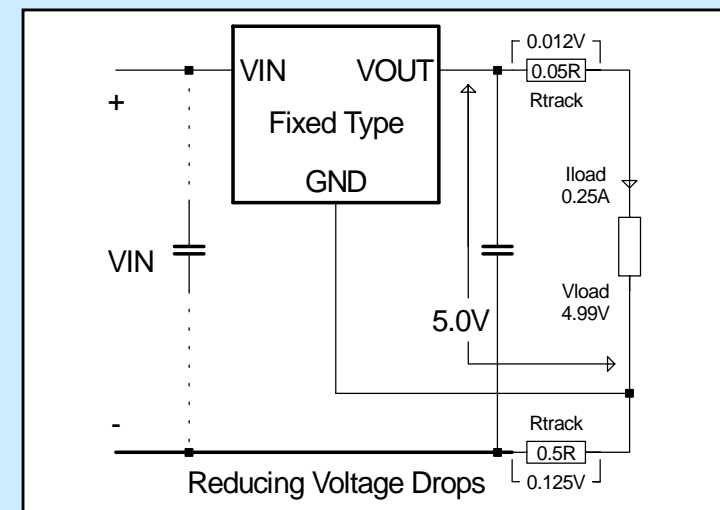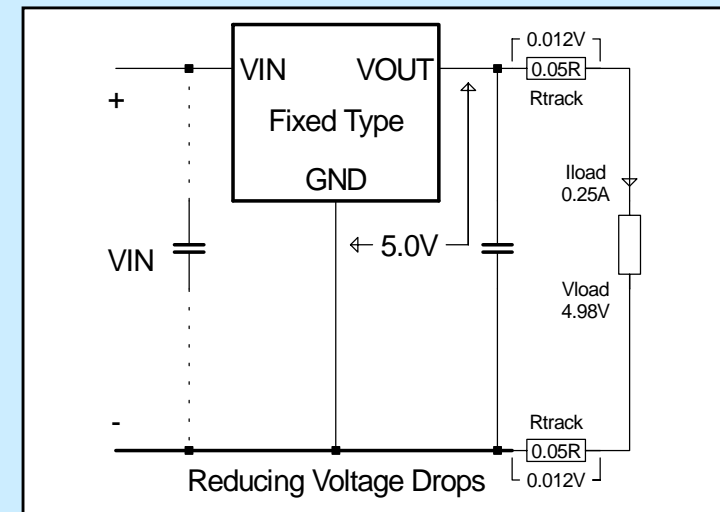- Method 1
Reduce Track Lengths from VReg. to Load
- Method 2
Maximise Track Widths - Reduces ohms/inch
- Method 3
Return Regulator GND Connection direct to the Load GND Connection
NOTE: only compensates for drops in the 0V line



Line Transient Response

• Line Transients

Change of V_{OUT} if V_{IN} changes suddenly

Regulator unable to cancel Fast Edges & HF

Line Transients can be caused by Back-EMF

Feeds through Regulator to CPU Supply

- sometimes with little, if any, attenuation
- mild cases could cause random ADC Conversion errors
- a bad case could lead to CPU brown-outs

• Possible Solutions

Choose a Regulator with a better Spec.



- the LM317 shown is not good in this respect
- the LM1117 is somewhat better

Fit Tantalum Capacitors to Input and Output

Reduce the Amplitude of Incoming 'Spikes'

Add a filter close to the regulator input

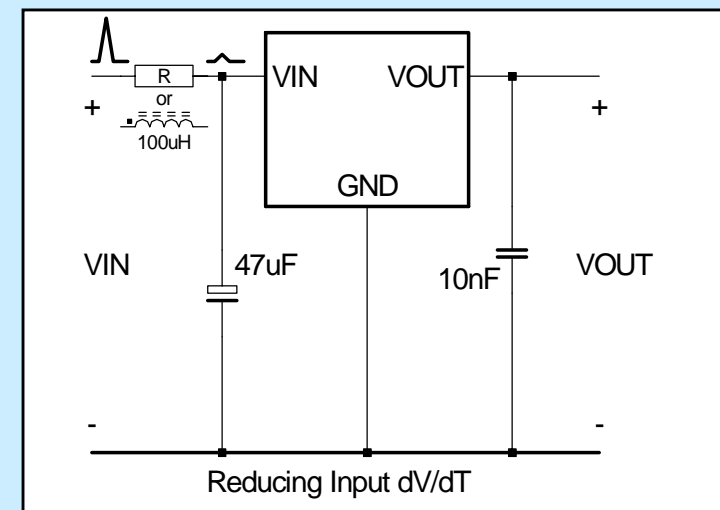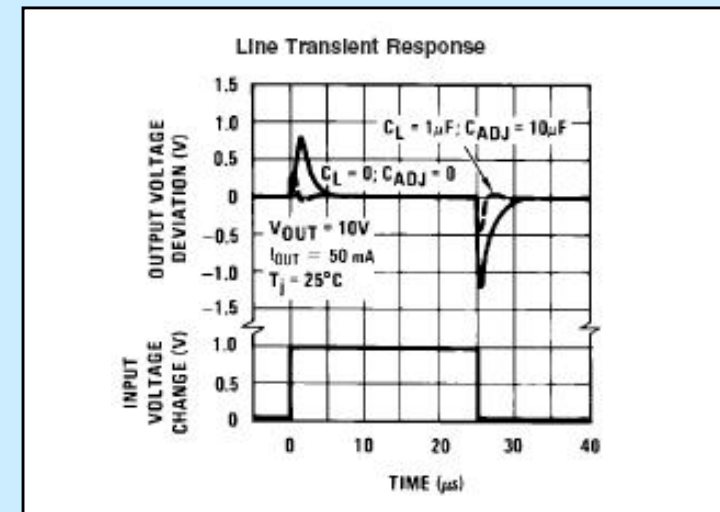- inductor gives best performance for high load currents
- resistor only suitable for low load currents - V_{DROP}



Load Transient Response

• Load Transients

Change of V_{OUT} if I_{LOAD} changes suddenly

Regulator unable to cancel Fast Edges

Load Transients can be caused by operation of Infra-Red Sensors

Feeds directly onto CPU Supply

- mild cases could cause random ADC Conversion errors
- a bad case could lead to CPU brown-outs

• Possible Solutions



Choose a Regulator with a better Spec.

- the LM317 shown is not good in this respect
- the LM1117 is somewhat better

Fit a Tantalum Capacitor directly to Output



- larger capacitor values generally give better results

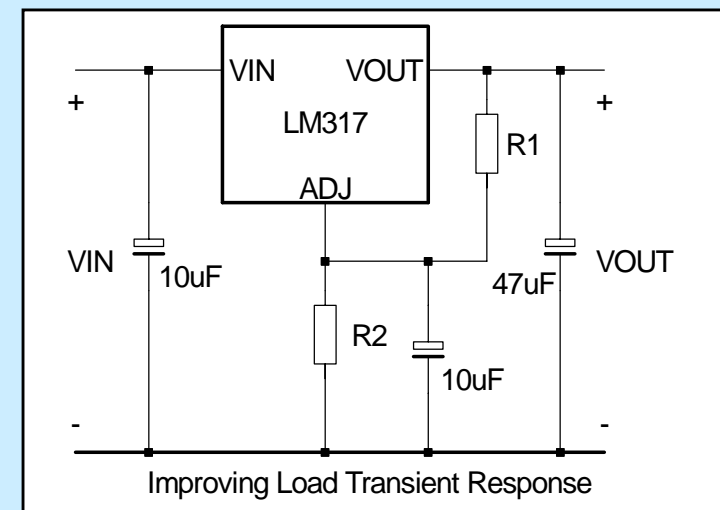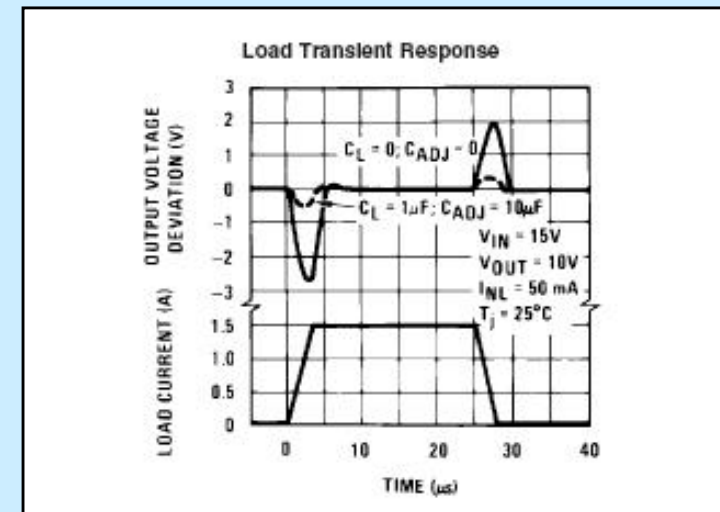For the LM317/ LM1117 fit a capacitor to the Adjustment Pin - say 10uF



Output Capacitor ESR

- A bit of an Esoteric Subject but it is important for LDO Regulators
- Equivalent Series Resistance
Capacitors have a small Internal Resistance
They also have a small Internal Inductance
- Lower Diagram shows the Range of tolerable ESR vs Load Current for LP2980 LDO: $C_{OUT} = 10\mu F$
- Capacitor Choice
 - Generally any Tantalum is OK
 - Low Value Al. Elecs. ESR may be too high
 - Beware of Multi-Layer Hi-Capacity Ceramics - they can have very low ESR values

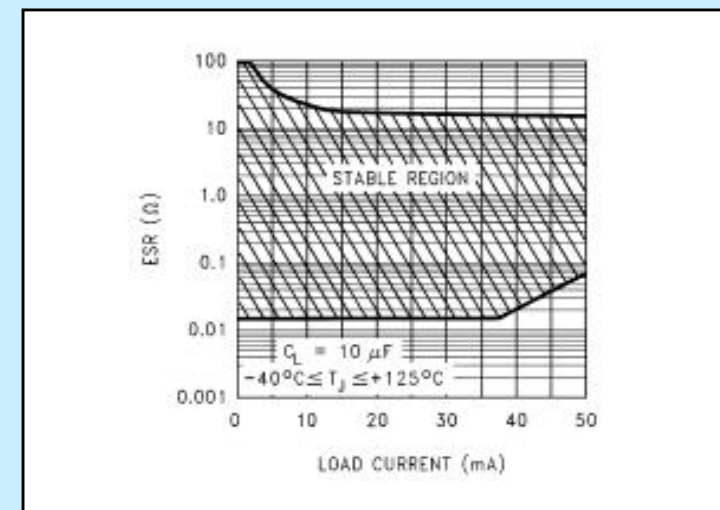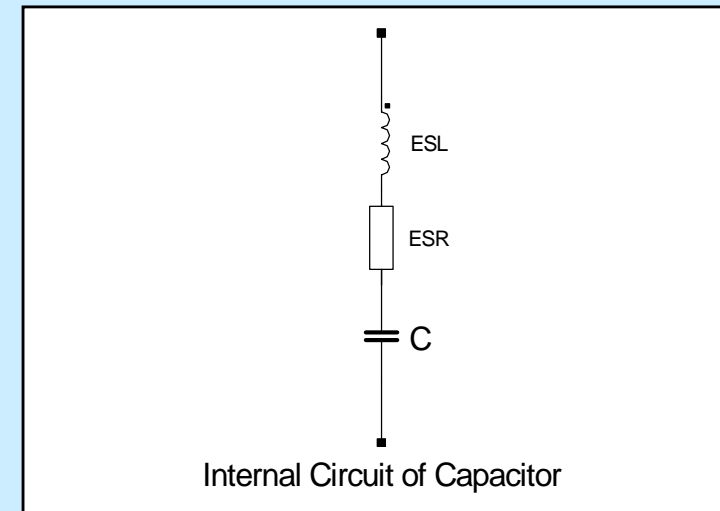



Ground (or Quiescent) Current

- Another Esoteric Subject but it is important for LDO Regulators

For the LM2940 regulator:

- Upper Graph
Shows I_{GROUND} vs I_{OUTPUT} @ $V_{\text{IO}} = 9\text{V}$
- 12mA @ $I_{\text{out}} = 0$ rising to 30mA @ $I_{\text{out}} = 1\text{A}$
- Lower Graph
Shows I_{GROUND} vs V_{IN} for various I_{OUT}
Of special note is the 1A curve:
- as V_{in} drops below 9V I_{q} rises rapidly
- using an LM2940 to provide 5V @ 1A from 2-Cell LiPo pack would not be satisfactory - 500mA probably OK

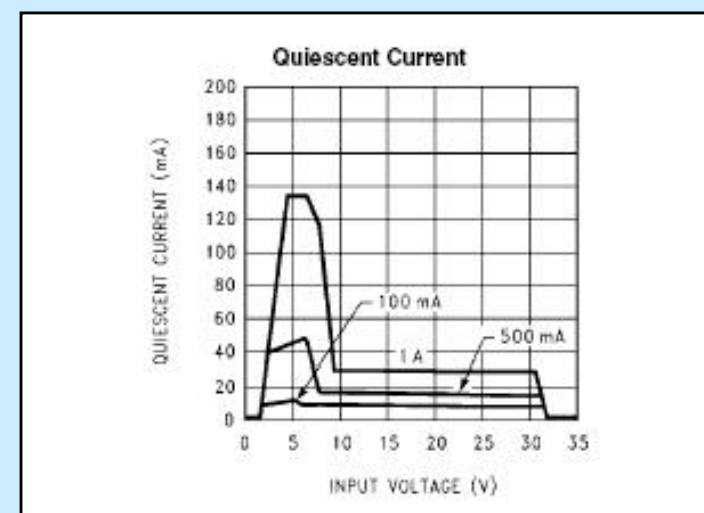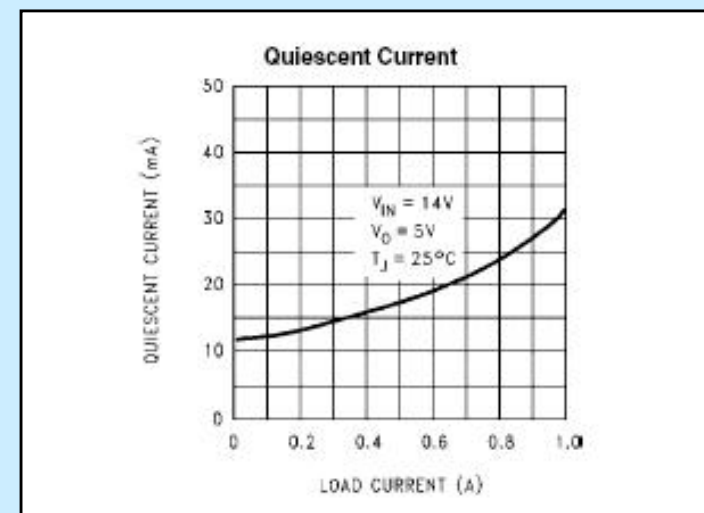NOTE: the graphs shown relate to the LM2940 5V/1A
- a first-generation LDO regulator
Second generation devices are better




Thermal Management - Sinking

- Linear Regulators Dissipate Heat - Sometimes Lots of It
 - using a 2-Cell LiPo pack to provide 5V @ 1A for Motors requires a regulator to dissipate 3W
 - this regulator needs a minimum heatsink of 30°C/W to ensure reliability, and even with this:
device junction temperature = $(3 \times 30) + 25^\circ\text{C} = 115^\circ\text{C}$
device case temperature approximately 100°C !

It's not usually convenient to put a conventional heatsink on a Mouse:

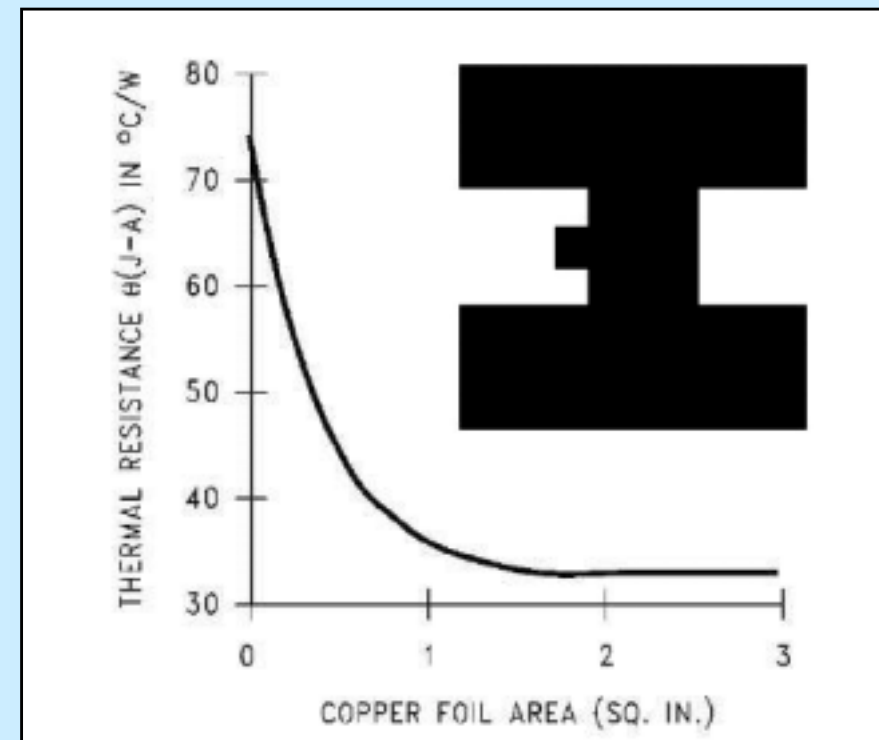- fabricate a 'heatsink' from copper zones on either, or both, sides
- can be used with:
 - TO220 TH devices lying down
 - TO252 SMD high-power devices
 - SOT223 SMD medium power devices
- can be any shape - avoid narrow webs
- more than 1 VREG can spread the load



Thermal Management - Sharing

- Method 1

Neither Regulator needs to be an LDO

- 5V device may need to be if V_{IN} can fall below 7.5V

$$P_{DISS\ 5V} = 3V \times 0.5A = 1.5W$$

$$P_{DISS\ 3V} = 5V \times 0.1A = 0.5W$$

- Method 2

3V (3.3V, 3.6V) Regulator must be an LDO



- 5V device may need to be if V_{IN} can fall below 7.5V

$$P_{DISS\ 5V} = 3V \times 0.6A = 1.8W$$

$$P_{DISS\ 3V} = 2V \times 0.1A = 0.2W$$

Consider the following when deciding:-

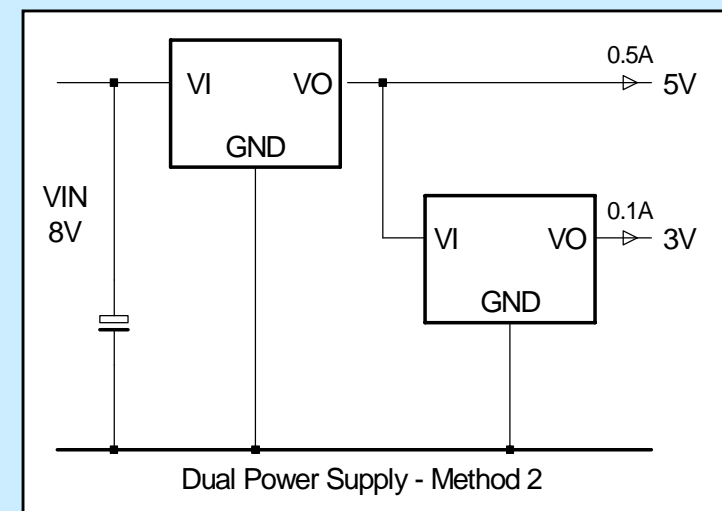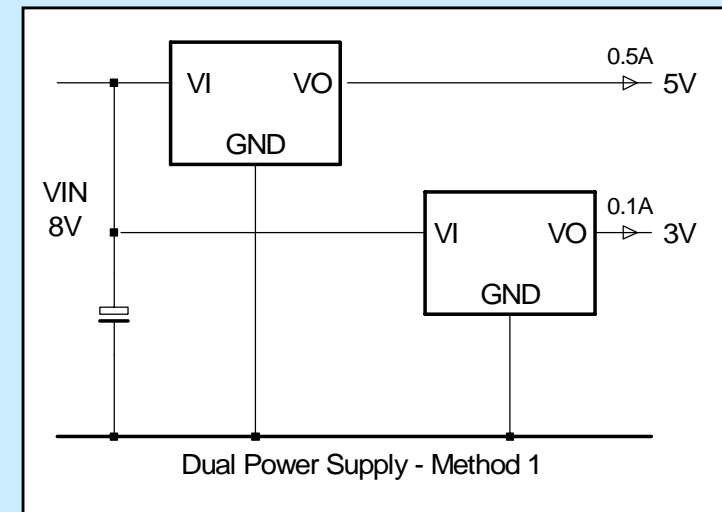
- carefully assess current drain on each supply
- relative locations of the voltage source and the load
- convenience of having a small local regulator for 3V
- dissipating the resulting extra power in the 5V device
- use the 'average' regulator dissipation - not the 'peak' (although using the peak value is conservative)



Monitoring The Supplies

Monitoring the Battery Voltage Provides an Early Warning

- as batteries discharge their Terminal Voltage reduces
 - eventually it drops low enough to prevent the regulators operating correctly
 - knowing this allows you to take some action - even if it just to shut the Mouse down
- Choose chain resistance to minimise power wastage - 0.5mA is OK
 - 100nF at ADC input filters HF noise
 - Choose RSET to utilise most of the ADC dynamic range
 - Set 'Trip Point' just above $V_{DROPOUT}$
 - but, if using an LDO, consider battery end-of-life terminal voltage - it can fall very quickly - and set Trip Point accordingly

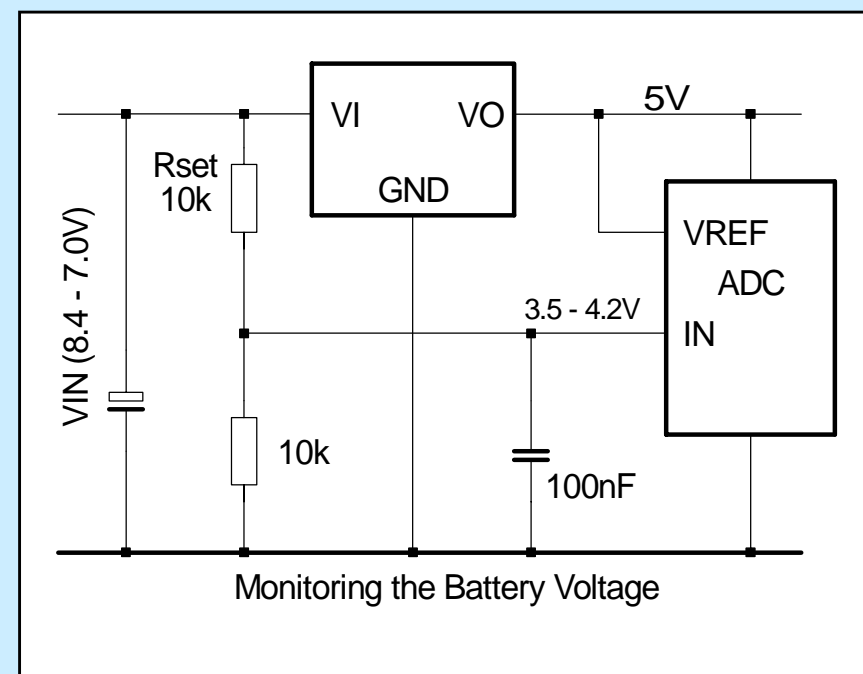

PCB Layout

This is where Science meets Art

A Well Designed Layout Provides:-

- A Robust Platform for the Circuit
- Operational Reliability
- Measurement Accuracy from Low Noise
- Low-Noise

We'll Take a Look At:-

- The Golden Rule
- Various Possibilities for Tracking Power and Ground Traces
- The Use of Local Regulators
- A Few PCB Format Options

Power and Ground Trace Rules

The Golden Rule

For Best Performance



ALL Power and Ground Traces **MUST** be Wide!

Wide Power & Ground Tracks

Left-Hand Wall Follower Power Board

- Bottom Side
 - Large Central Area is 0V (copper-fill technique)
 - Connects Front and Rear Areas Together
 - 'C' shaped area on RHS is +5V to Motors
 - Wide Track at RH End connects Batteries
- Top Side
 - Central Area at RHS is Regulator Heatsink
 - Central Wide Track is +5V to Sensors
 - Upper/Lower Wide Tracks connect Batteries

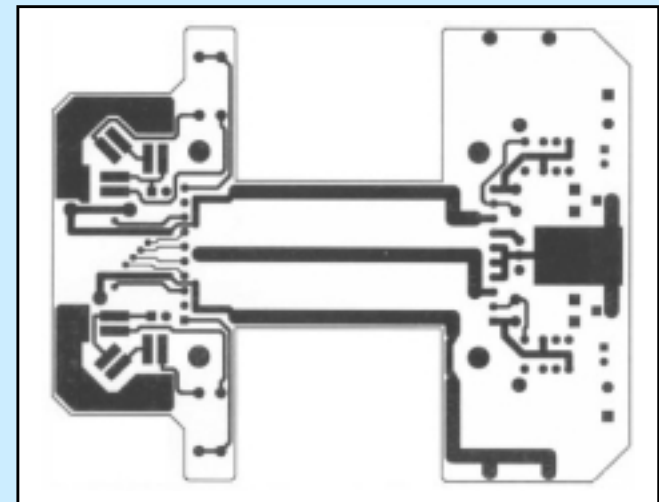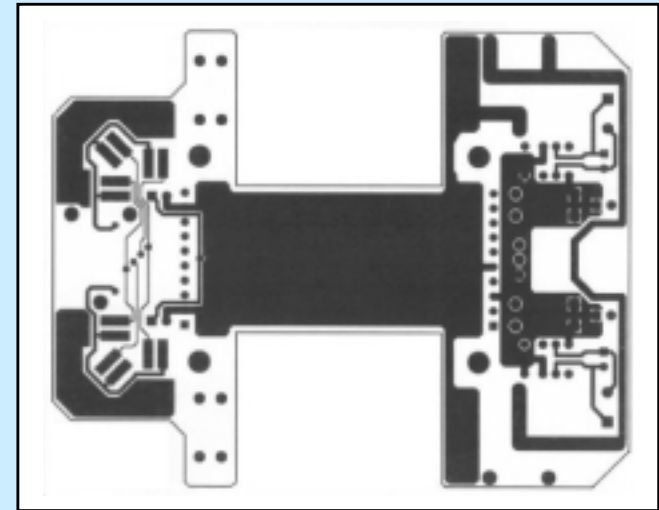NOTE: The 'L' shaped copper areas at left are Light Shields for the Infra-Red Sensors



Power and Ground Trace Rules

Another Golden Rule



For Best Performance

All Power and Ground Traces NEED NOT be Wide!

Local High-Current Circuits

Infra-Red Sensor Circuit




- High-Current Capacitor Discharge
 - LED Current determined by R_{DROP}
 - Can be as high as 200mA - wide tracks
 - R_{ISO} limits current provided by main supply
 - Capacitor provides almost all energy
 - High Current path is very small and local
 - Return Current to Main Supply also limited
- Low-Current Capacitor Charge
 - Charging Current determined by V_{DROOP}
 $(5.0V - 4.9V) / 10R = 10mA \text{ max}$
 - Charge Current path may be extensive and laid with narrow tracks with no detrimental effect as current is low

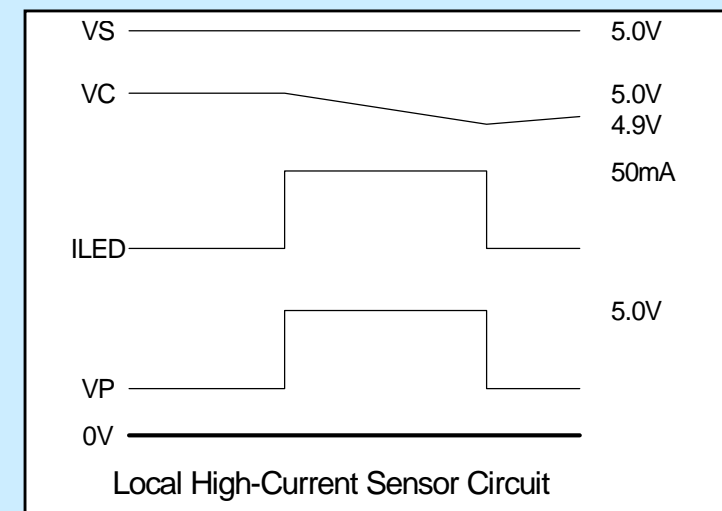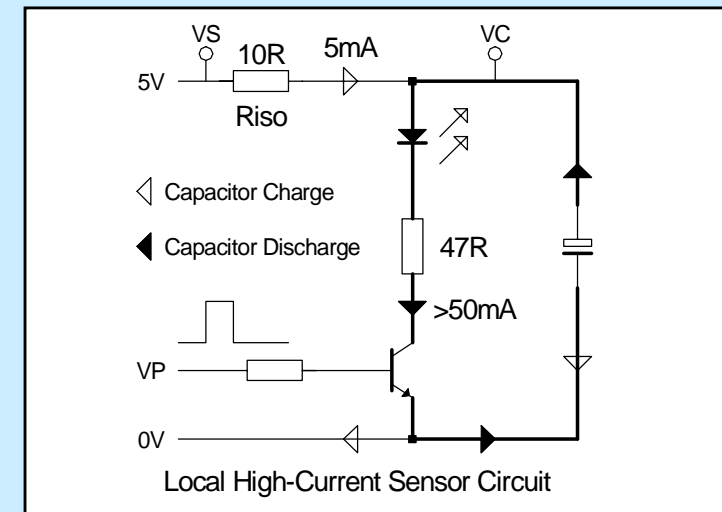

Tracking Power & Ground Traces

- Copper Flood (Fill) or Plane
 - Provides the lowest resistance
 - Provides the lowest inductance
 - Usually permits 'automatic' connectivity
 - Allows current paths to be determined if Zone Boundary is suitably described
- Star Points
 - Route each circuit's Return separately to 0V
 - Minimises Coupling of 0V-Line Interference
 - Permits separation of analogue and digital
- Track Necking
 - Each track is a series of small sections
 - wide tracks are low resistance sections
 - narrow tracks are high resistance sections
 - Maximise track width where possible
 - reduce it where necessary

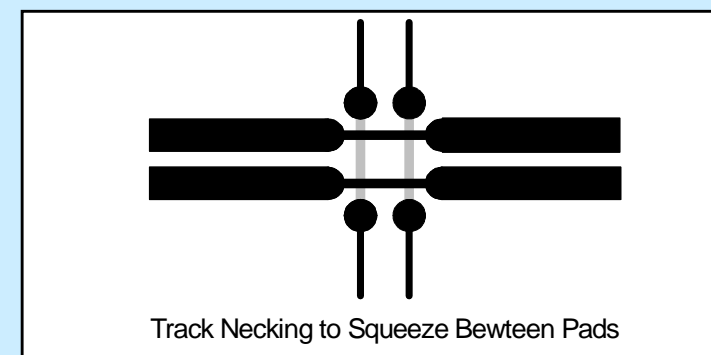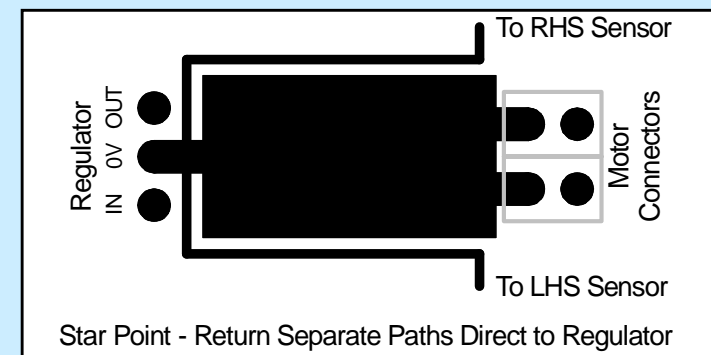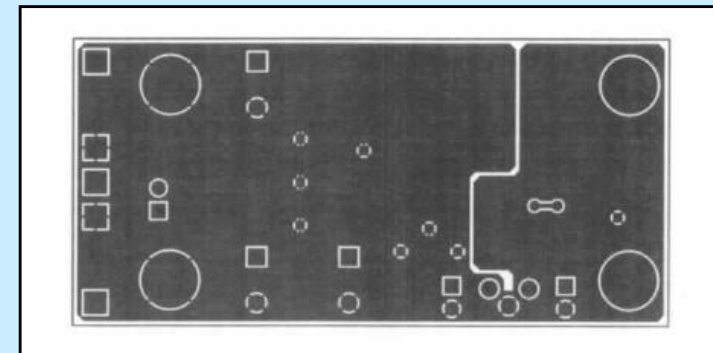Applies equally well to Power Traces as to Ground




Use Local Regulators

Local Regulators Can Provide:

- Accurate Supply where it's Needed
- Lower Supply-borne Noise Levels
(susceptibility and emissions - works both ways)
- Simplified PCB Tracking
(low current supply feeds can be narrow)
- Special Odd-Value Supply Voltages
(ADC References, Motor and/or Sensor Supplies)

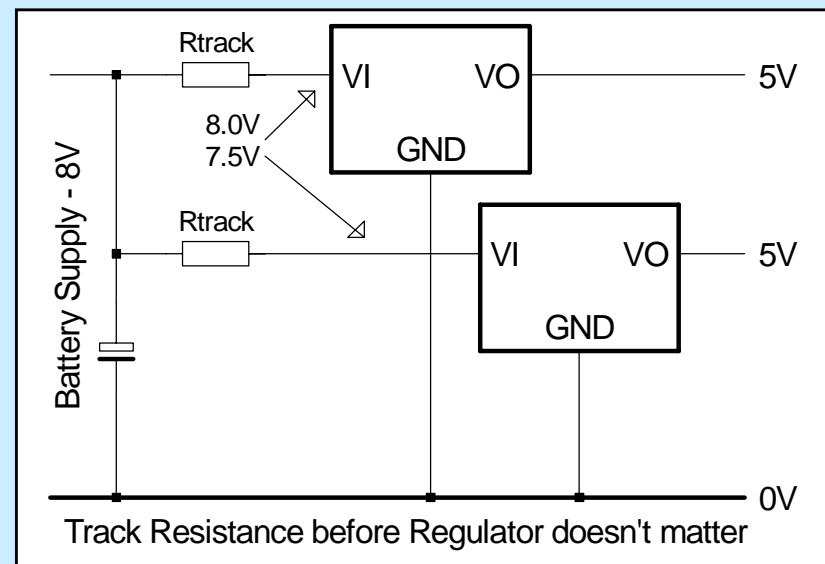For Low-Current Supplies the Regulator can be in a small package such as SOT23



Track Resistance on regulator supply side is not important - provided that the input voltage to the regulator does not fall below the level required to maintain regulation ($V_{OUT} + V_{DROP-OUT}$)

Single or Multi-Layer Boards ?

Single-Sided Board


- Copper Layer on One Side Only - Cheapest
- Power, Ground and Signals all on One Layer
- Difficult to Route anything but Simple Layouts
almost always needs 'jumper links' - takes space

Double-Sided Plated Thru Hole

- Copper Layers on Both Sides
- Layers can be Joined using Plated Thru Vias
- Can Separate Power & Ground and Signals
- Routing is Easier due to 'Escape Routes'
- Reasonably Priced from Specialist Suppliers

Multi-Layer Board

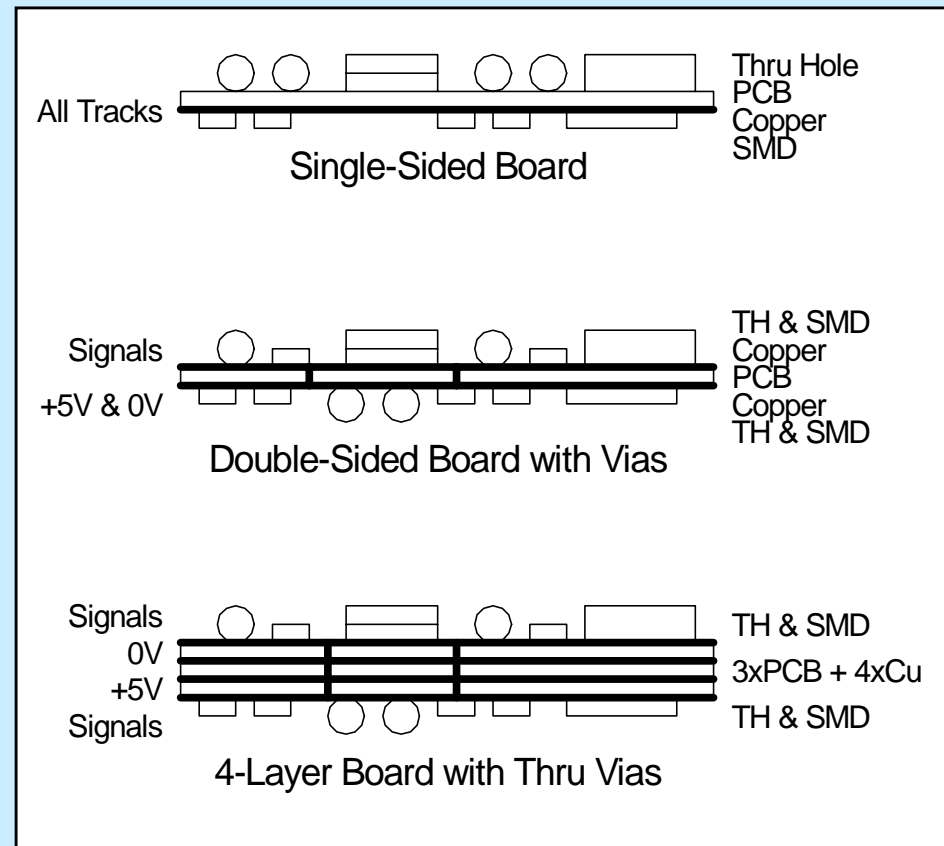- 4 < or more > Copper Layers in a Sandwich
- Permits Extensive use of Copper Planes
- Can Dedicate Layers to Power & GND Planes
- Rather Expensive
but that's OK if you happen to know an MP!



Determining Track Widths

- PCB Copper Foil is specified as the 'Weight of Copper per Sq. Foot'
 - Typical Weights are 0.5, 1 and 2 ounces - 1oz being most common
 - Heavier Copper gives greater Thickness - Lower Resistance
- (Note that, even in this metric age, values are still usually given in Imperial Units)

Common PCB Statistics

- Copper Weight 1oz
- Copper Thickness 1.37mils

The table gives 'specific resistance' and typical current carrying capacity for various 1oz weight track widths

Scale as appropriate for 0.5oz and 2oz

Width (in)	Width (mm)	Ohms/Inch	Max Current
0.005	0.125	0.100	0.5A
0.010	0.250	0.050	0.9A
0.015	0.375	0.033	1.2A
0.020	0.500	0.025	1.5A
0.025	0.625	0.020	1.7A
0.050	1.250	0.010	2.8A
0.100	2.500	0.005	4.5A

Typical 1oz-Copper PCB Statistics

In Summary

- Know your Circuit's Supply Voltage Requirements
- Know the Range of Battery Voltage:
 - use maximum to calculate regulator power dissipation
 - use minimum to determine regulator type - Standard or LDO
- Carefully read the Regulator's Datasheet
 - try to understand what it is telling you
 - try to fathom out what it is NOT telling you
- Determine Regulator arrangement in Multi-Supply Systems
 - is it better to power both direct from the battery - or one from the other
- Estimate the Power Dissipation in each Regulator
- Estimate the size of any necessary Heatsinking arrangement
 - a 0.5 sq.in copper-zone sink can safely dissipate about 1W - maybe 1.5W
 - a wide 0V track can do double-duty - acting as a heatsink too
- Plan 0V & Power Routing early in the layout process
 - signal tracks having to 'hop over' power tracks is better than the other way round
- Don't be afraid to change the Schematic - even during Layout
 - sometimes adding an extra sub-circuit or component can ease a layout problem

Power & Ground Systems

That's all Folks